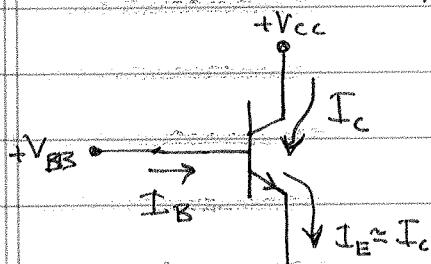


## Notes on the Common-Emitter Amplifier

- The Bipolar Junction Transistor (BJT), when its terminals are properly biased, provides large current gain.

$$I_c = \beta I_B \quad \text{where } \beta \approx 100$$




The base-emitter junction is forward-biased,  $V_{BE} > 6V$   
 The base-collector junction is reverse-biased.  
 $V_{CC} \gtrsim V_{BB}$


(n-p-n transistor used throughout)

- Resistors can be used to convert currents into voltages.

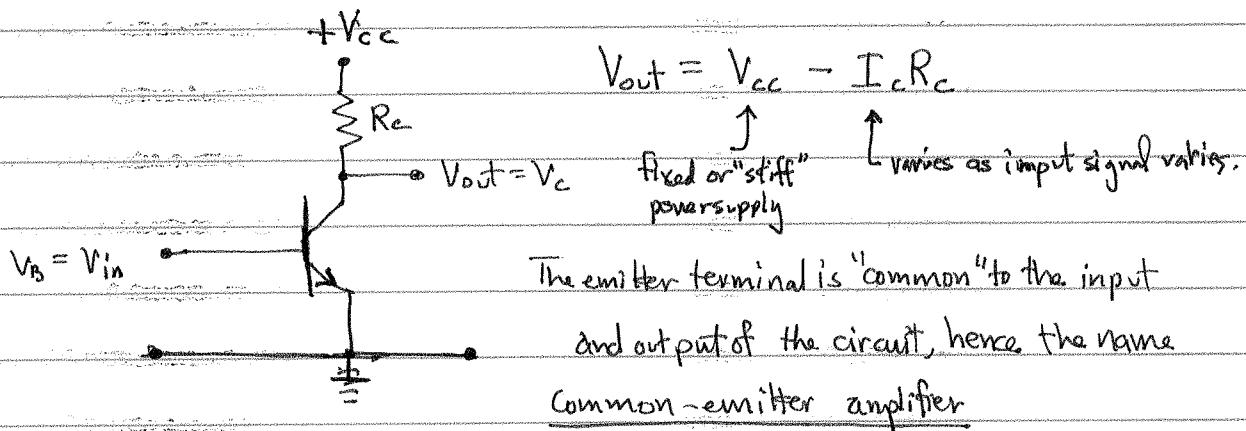In the case of the common-emitter amp, the output voltage is taken from the collector and a resistor <sup>is used</sup> between the collector power supply and the transistor.



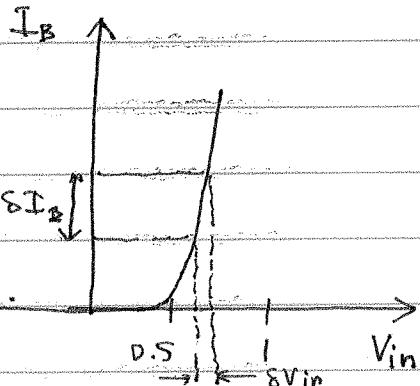- The base current is very sensitive to the input voltage ... it is a pn junction in the forward-biased regime.



Shockley eq.  $I_B = I_s (e^{\frac{V_B}{V_T}} - 1)$

$I_B = I_s e^{\frac{V_B}{V_T}}$  ↑ ignore in forward bias  
 regim

If  $V_B = V_{BB} + \delta V_B$   
 ↑ signal  
 ↓ D.C. bias

$$I_{Bq} + \delta I_B = \left( I_s e^{\frac{V_{BB}}{V_T}} \right) e^{\frac{\delta V_B}{V_T}}$$

↑ change in base current due to signal

"quiescent" base current

expand this for small signals  
 $\delta V_B \ll V_T = 26 \text{ mV}$   
at 300 K

$$I_{Bq} + \delta I_B = \left( I_s e^{\frac{V_{BB}}{V_T}} \right) \left( 1 + \frac{\delta V_B}{V_T} \right)$$

$I_{Bq}$  (Note: Both  $I_s$  and  $V_T$  are temperature-dependent at fixed  $V_{BB}$ ).

$$\text{So... } \delta I_B = I_{Bq} \frac{\delta V_B}{V_T}$$

The base to emitter junction  
"looks like" at resistor to small variations

in the input voltage...

[Order of magnitude  $r_{\pi} \approx \frac{26 \text{ mV}}{0.1 \text{ mA}} \sim 2.6 \text{ k}\Omega$ ]

$$r_{\pi} = \frac{V_T}{I_{Bq}}$$

Horowitz-Hill call

~~the~~ Ebers-Moll  
resistance  $r_e = \frac{r_{\pi}}{\beta}$

s.t.  $r_e = \frac{V_T}{I_{eq}}$

$$\delta I_c = \beta I_{Bq} \cdot \frac{\delta V_B}{V_T} \quad \text{or} \quad \frac{\beta \delta V_B}{r_{\pi}}$$

$I_{eq}$  quiescent collector current

- Changes in the output voltage due to changes in the input voltage  
→ Amplifier gain

$$V_{outq} + \delta V_{out} = \underbrace{V_{cc} - I_{eq} R_c}_{V_{outq}} - R_c \delta I_c$$

$V_{outq}$  quiescent D.C. output voltage

$$\text{So } \delta V_{out} = -R_c \delta I_c = -\frac{R_c \beta}{r_{\pi}} \delta V_{in}$$

$\uparrow = \delta V_B$


Voltage Gain  $A_V = \frac{\delta V_{out}}{\delta V_{in}} = \frac{-R_c \beta}{r_{\pi}}$

Positive swing in  $\delta V_{in}$  increases  $\delta I_B$  and  $\delta I_c$

making  $\delta V_{out}$  swing negative

-2- → Inverting amplifier.

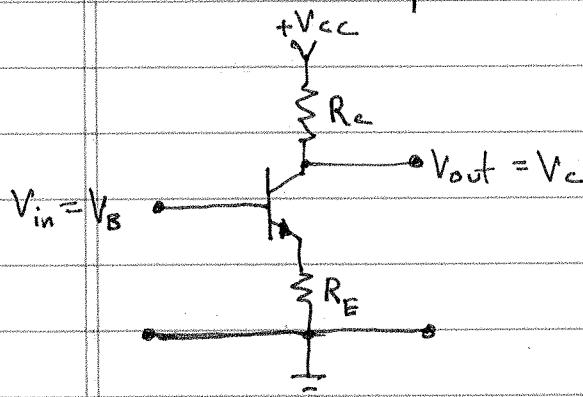- The gain obtained on the previous page depends on the current gain parameter,  $\beta$ , for the transistor, and on the temperature (and quiescent operating point)-dependent effective resistance,  $r_{\pi}$ . To make the amplifier performance less dependent on these unreliable factors, add a resistor to the emitter portion of the circuit.



This addition constitutes an application of "negative feedback" and is a sacrifice of gain for other performance characteristics.

Now it is the voltage difference between the base and emitter (no longer grounded) that determines the collector current (and hence the output voltage)

$$\delta I_B = \frac{1}{r_{\pi}} \cdot (\delta V_{in} - \delta V_E)$$

$\uparrow$  base

The emitter voltage is  $V_E = I_E R_E = (\beta + 1) I_B R_E$

$$\delta V_E = (\beta + 1) R_E \delta I_B$$

$$\delta I_B = \frac{\delta V_{in}}{r_{\pi}} - \frac{(\beta + 1) R_E}{r_{\pi}} \delta I_B$$

$\uparrow$  negative feedback

.. reduces the magnitude of the change in  $I_E$

Solve for  $\delta I_B$

$$\delta I_B \left( 1 + \frac{(\beta + 1) R_E}{r_{\pi}} \right) = \frac{\delta V_{in}}{r_{\pi}}$$

$$\delta I_B = \frac{\delta V_{in}}{r_{\pi} + (\beta + 1) R_E} \rightarrow \delta I_C = \beta \delta I_B = \frac{\beta \delta V_{in}}{r_{\pi} + (\beta + 1) R_E}$$

From the previous page...  $\delta V_{out} = -R_c \delta I_c$  so..

$$\delta V_{out} = \frac{-\beta R_c}{r_T + (\beta+1)R_E} \delta V_{in}$$

and the gain is...

$$A_v = \frac{-\beta R_c}{r_T + (\beta+1)R_E}$$

If  $(\beta+1)R_E \gg r_T$  and  $\beta \gg 1$  then this reduces to...

$A_v = \frac{-R_c}{R_E}$  Independent of transistor characteristics  
and temperature!

need  $R_E > 26 \Omega \left( \frac{r_T}{\beta+1} \right)$

- Establishing the quiescent operating point for the common-emitter amplifier: In order to amplify the A.C. component of the input voltage, there must be a steady or quiescent current through the transistor ... the transistor must be "on". The output is taken at the collector which has a quiescent voltage...

$$V_{cq} = V_{cc} - I_{cq} R_c$$


Or, the quiescent collector-emitter voltage is...

$$V_{CEq} = V_{cc} - I_{cq} R_c - I_{Eq} R_E \approx V_{cc} - I_{cq} (R_c + R_E)$$

for large  $\beta$ .  $I_{cq} \approx I_{Eq}$

This represents a linear relationship between  $I_{cq}$  and  $V_{CEq}$ ,

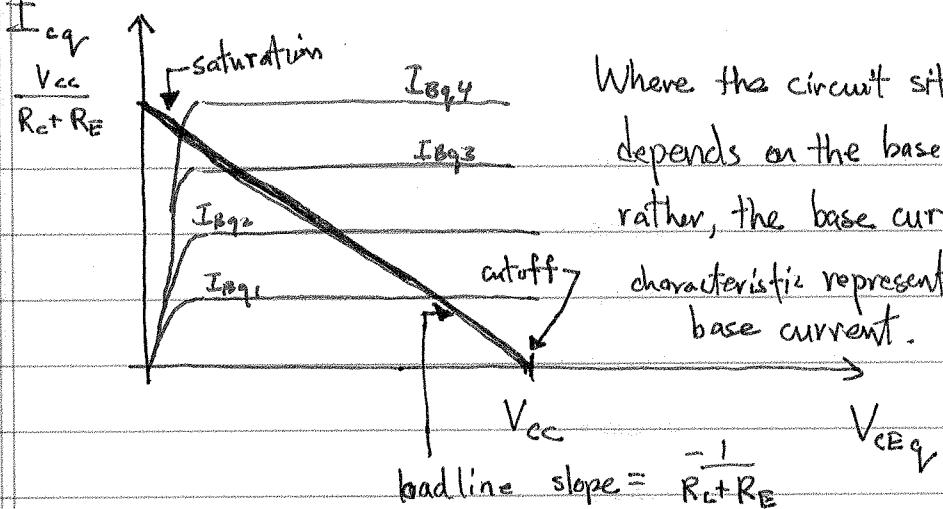and is the collector circuit "load line".




Where the circuit sits on the load line depends on the base-to-emitter bias or rather, the base current. Each horizontal characteristic represents a different quiescent base current.

$$\text{load line slope} = -\frac{1}{R_c + R_E}$$

The optimal position for the Q-point is near the middle of the load line in order to allow maximal and symmetric ~~sym~~ oscillation about that point without distorting the output (due to either cutoff or saturation).


- Power limit: Most of the power dissipated in the transistor is localized to the region of ~~large~~ strong electric field associated with the reverse biased collector-base junction. Overall the dissipated power is (approximately)  $P = I_{Cq} V_{CEq}$

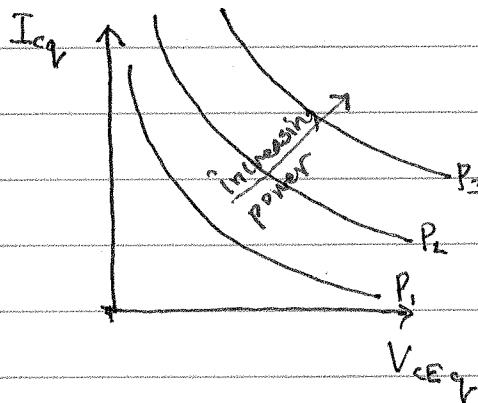Curves of constant power are hyperbolae in the graph of  $I_{Cq}$  vs.  $V_{CEq}$



The circuit elements  $V_{cc}$ ,  $R_c$ , and  $R_E$  should be selected so that the load line lies well below the ~~power~~ constant power contour associated with the maximum power dissipation in the transistor.

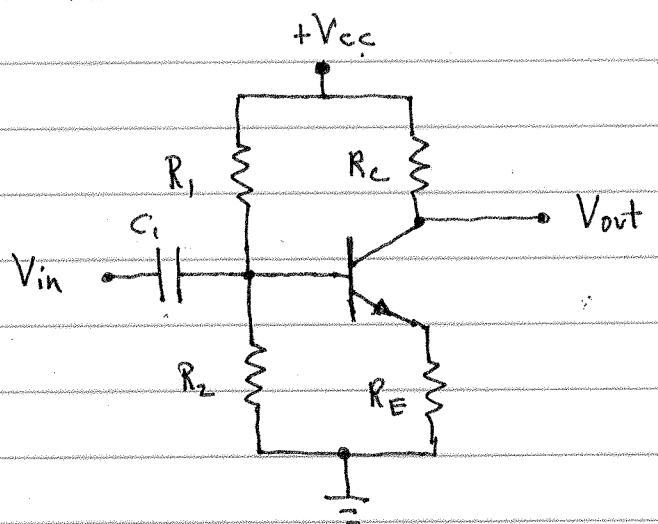- Four-resistor bias circuit: It is desirable to minimize the number of separate D.C. power supplies that are needed to establish the Q-point and render the circuit receptive to input signals. The standard method is to use the supply that provides  $+V_{CC}$  to also provide  $V_{BQ}$ , the quiescent base voltage, through a voltage divider.



$R_1$  and  $R_2$  form a voltage divider with input  $+V_{CC}$  such that its output,  $V_{BQ}$  ...

$$V_{BQ} = \frac{R_2}{R_1 + R_2} V_{CC} \approx \underbrace{I_{EQ} R_E}_{V_{EQ}} + 0.6 \text{ V}$$


forward-biased base to emitter junction voltage.

For this to hold, the base current  $I_{BQ}$  must be small compared to the current through  $R_1$  and  $R_2$ .

The input coupling capacitor  $C_1$  is necessary, in order to avoid perturbing the Q-point when the signal source is attached.

The amplifier will therefore operate on (i.e. amplify) only the A.C. part of the input signal. Stay tuned for analysis of frequency-dependent effects.

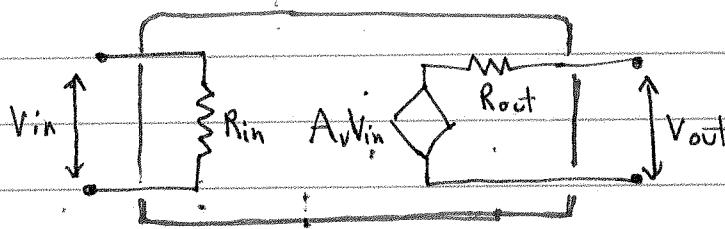- **Input Impedance**: ~~Value~~ is an important characteristic for an amplifier and one we generally like to be large for voltage amplifiers. This reduces the loading of the signal source. When considering these quantities, it is helpful to view the circuit of interest in the following effective representation




In general input and output resistors should be replaced with impedances that can have imaginary components (capacitance, usually).

We are here neglecting the coupling capacitor...

The input is A.C. at sufficiently high frequency that the impedance of the capacitor is negligible.

The input resistance is then ...  $R_{in} = \frac{\delta V_{in}}{\delta I_{in}}$

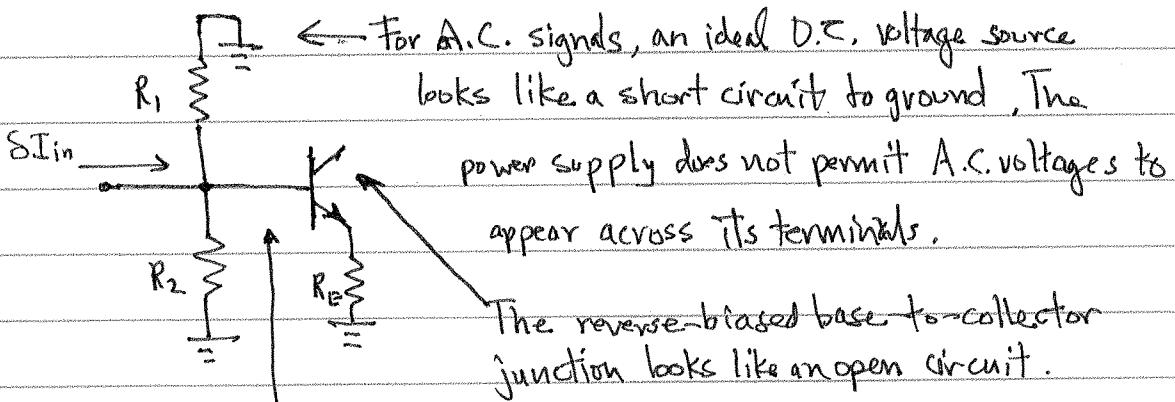For our circuit, the input current has three parallel paths to ground:




The effective input impedance of the path to the base of the transistor can be obtained from the equation on the bottom of page 3.

$$R_{in+} = \frac{\delta V_B}{\delta I_B} = r_{\pi} + (\beta + 1)R_E$$

So, the overall input resistance of the amplifier is...

$$R_{in} = R_1 \parallel R_2 \parallel R_{int}$$

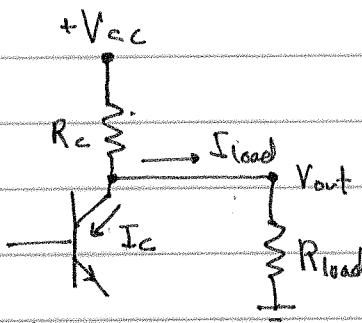The output resistance can be predicted from the collector/output circuit



When a load is attached to the output, additional current must flow through  $R_c$  to supply the load.

The collector current is not (much) affected by the load as long as the  $V_{out}$  output is not dragged down (loaded down) so much that the transistors Q-point is brought to saturation.

$$\text{So... } V_{out} = V_{cc} - (I_c + I_{load})R_c$$

and


$$R_{out} = \frac{-\delta V_{out}}{\delta I_{out}} = R_c$$

Since the output drops as the load current increases

- The desire to maximize  $R_{in}$  and minimize  $R_{out}$  for a voltage amplifier must compete with (or be traded off against) other amplifier characteristics like gain, bandwidth, and stability.

- Frequency response :

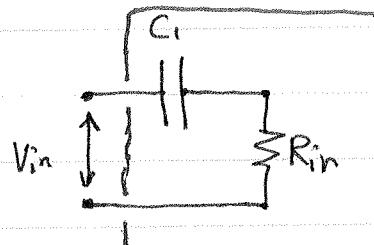
- Low frequency roll-off : The input coupling capacitor in the common-emitter amplifier design forms a RC high pass filter with the input resistance (p.8).



The low frequency half-power frequency is therefore...

$$f_{lo} = \frac{1}{2\pi R_{in} C_1}$$

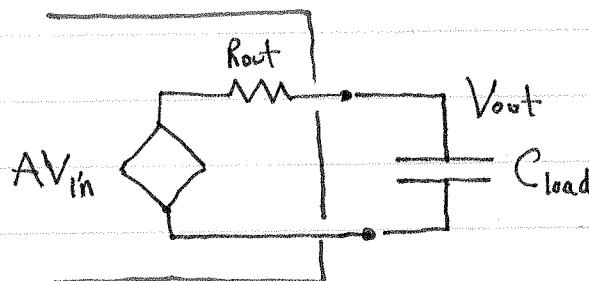- High frequency roll-off : There are a number of possible effects that can lead to low pass filtering or high frequency roll-off in the gain. The simplest one to understand is one that arises when the load attached to the output of the amplifier has capacitance. Then the output resistance and the load capacitance form a RC low pass filter (p.8)



The high frequency half-power point associated with load capacitance is...

$$f_{hi} = \frac{1}{2\pi R_{out} C_{load}}$$


If the load is a coaxial cable (RG-58) connected to an oscilloscope, then

$$C_{load} \approx 30 \text{ pF/ft.} \times L \text{ (ft.)} + C_{scope}$$

<sup>t typically ~ 20 pF</sup>

- Enhancing the gain using a bypass capacitor:

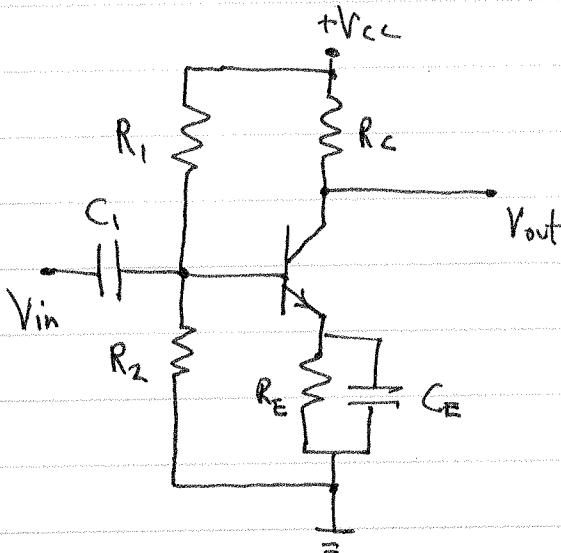For A.C. signals, the midband gain can be enhanced by putting a capacitor in parallel with  $R_E$ . The capacitance should be chosen so that the impedance of the capacitor ( $\frac{1}{\omega C}$ ) is small compared to  $R_E$  at the frequencies of interest.



The input impedance of the transistor "looking into" the base is now frequency dependent and the low-frequency roll-off will therefore be affected.

Referring to p.4, the gain can be expected to reach values limited by the following

$$A_{V, \text{Max}} = -\beta \frac{R_c}{r_T}$$

where  $\frac{r_T}{\beta} \approx 26 \Omega$  at room temp.  
with  $\beta \approx 100$   
 $I_{Cq} \approx 1 \text{ mA}$