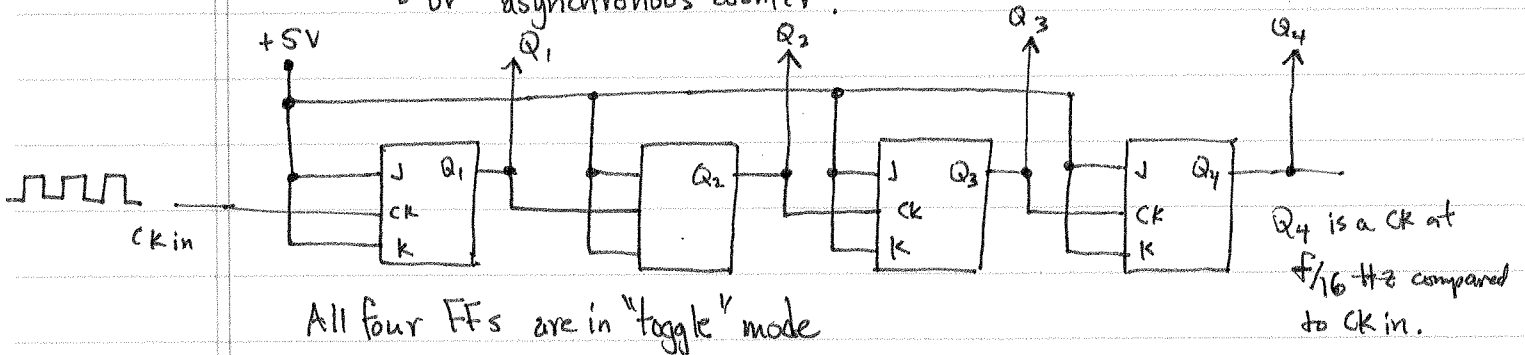



Notes on Digital Counters

- Four bit "ripple counter" uses 4 JK Flip-flops

↑ or "asynchronous" counter.



 Timing diagram ... the changes in the output 4-bit number "ripple" through the register due to the finite response time of the flip-flops.




Read output states with Q_4 as MSB and Q_1 as LSB...

CK pulse	Q_4	Q_3	Q_2	Q_1
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

↓ Binary counting from 0 to 15. before repeating


• A Divide-by-five Synchronous Counter

 

All FF's triggered on same CK... synchronous

CK pulse	J ₁	K ₁	FF ₁ state	J ₂	K ₂	FF ₂ state	J ₃	K ₃	FF ₃ state	Q ₃	Q ₂	Q ₁	binary count from 0 to 4
0	1	1	T	0	0	M	0	1	R	0	0	0	from 0 to 4
1	1	1	T	1	1	T	0	1	R	0	0	1	
2	1	1	T	0	0	M	0	1	R	0	1	0	
3	1	1	T	1	1	T	1	1	T	0	1	1	
4	0	1	R	0	0	M	0	1	R	1	0	0	
5	1	1	T	0	0	M	0	1	R	0	0	0	repeat

 To get a nearly synchronous binary counter from 0 to 9 (\div by 10 counter) add a divide by 2 to the front-end driving the CK input to the \div 5 counter above.




This FF will toggle every CK cycle... giving the f/5 counter a clock that is $f/2$...

CK ₀	Q ₃	Q ₂	Q ₁	Q ₀
0	0	0	0	1
1	0	0	1	0
2	0	0	1	1
3	0	1	0	0


etc...

When output gets to 1001, it will repeat ... 0 to 9 counter !!

• Seven-segment LED display

 

Each segment is a light-emitting diode

 

emits light when forward-biased
... conducting.

Anodes are held HI. Segment lights up when cathode is LO

Decimal (K_0)	Binary-Coded Decimal ($\div 10$) Counter				7-segment display cathode state							Display
	Q_3	Q_2	Q_1	Q_0	A	B	C	D	E	F	G	
0	0	0	0	0	0	0	0	0	0	0	1	
1	0	0	0	1	1	0	0	1	1	1	1	
2	0	0	1	0	0	0	1	0	0	1	0	
3	0	0	1	1	0	0	0	0	1	1	0	
4	0	1	0	0	1	0	0	1	1	0	0	
5	0	1	0	1	0	1	0	0	1	0	0	
6	0	1	1	0	1	1	0	0	0	0	0	
7	0	1	1	1	0	0	0	1	1	1	1	
8	1	0	0	0	0	0	0	0	0	0	0	
9	1	0	0	1	0	0	0	1	1	0	0	



BCD-to-7 segment decoder

logic gates!!