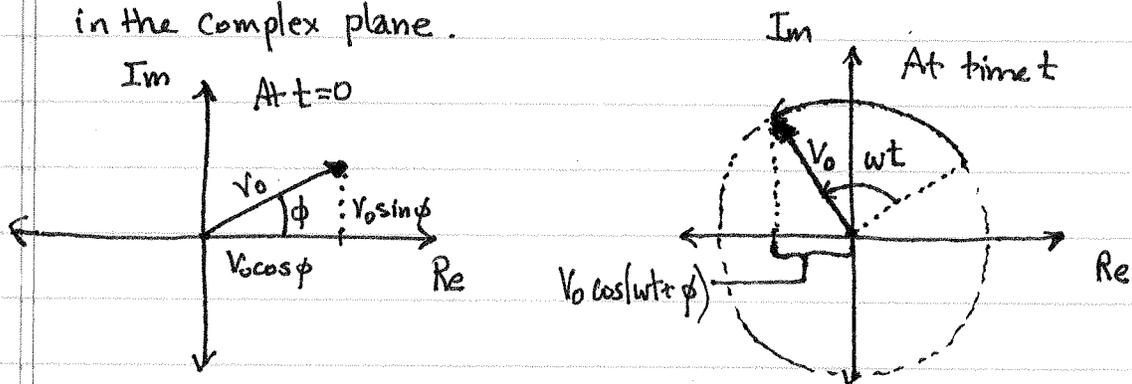


Notes on  
Complex Impedance and Phasors


- Analysis of A.C. circuits is aided by the use complex exponential functions and "phasors" to represent oscillating circuit quantities.
- Recall Euler's formula:  $e^{j\theta} = \cos\theta + j\sin\theta$       $j = \sqrt{-1}$
- Represent oscillating quantities (like voltage):  $\tilde{V}(t) = V_0 e^{j\omega t} = V_0 \cos\omega t + jV_0 \sin\omega t$   
 the real part of this function is the value that would be measured at time  $t$ .
- A phase shift can be incorporated into the (complex) amplitude:  

$$\tilde{V}(t) = V_0 e^{j(\omega t + \phi)} = V_0 \cos(\omega t + \phi) + jV_0 \sin(\omega t + \phi)$$

$$= V_0 e^{j\phi} e^{j\omega t}$$
 or  $\tilde{V}(t) = \tilde{V}_0 e^{j\omega t}$      where  $\tilde{V}_0 = V_0 e^{j\phi} = V_0 \cos\phi + jV_0 \sin\phi$
- Complex oscillating quantities can be visualized as vectors rotating in the complex plane.



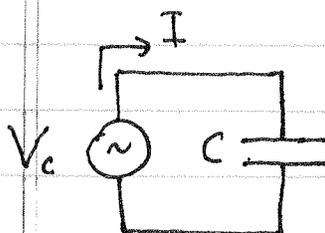- Relation between voltage (across) and current (through) a capacitor:



Kirchhoff loop rule:  $V_c - \frac{Q}{C} = 0$

Take derivative:  $\frac{dV_c}{dt} - \frac{1}{C} \frac{dQ}{dt} = 0$

or ...  

$$-|- \quad \frac{dV_c}{dt} = \frac{I}{C}$$

Replace  $V_c$  with  $\tilde{V}_c$  and  $I$  with  $\tilde{I}$  ... complex exponential functions.  
 Then..  $\frac{d\tilde{V}_c}{dt} = j\omega\tilde{V}_c$  from derivative of exponential function.

Substitute in...  $j\omega\tilde{V}_c = \frac{1}{C}\tilde{I}$  or...  $\tilde{V}_c = \frac{1}{j\omega C}\tilde{I} = \underbrace{\frac{-j}{\omega C}}_{\tilde{Z}_c}\tilde{I}$

- Impedance of a capacitor:  $\tilde{Z}_c = \frac{-j}{\omega C}$   
 analogous to resistance since it relates current to voltage.  
 But... is large at low frequency and small at high frequency.
- In general, a linear circuit element (or the effective combination of elements) has a complex impedance, so that current and voltage are related by...



$$\tilde{V} = \tilde{I}\tilde{Z}$$

Complex but constant in time ... generally depends on frequency however. Units are ohms ( $\Omega$ ).

- Phasors for capacitor: choose to draw phasors at the instant when the phasor for the current  $\tilde{I}$  is on the positive real axis. Then  $\tilde{V}_c$  lies on negative imaginary axis...

$$\tilde{V}_c = \underbrace{\frac{-j}{\omega C}}_{\text{pure imaginary impedance}} \tilde{I}$$

↑ real

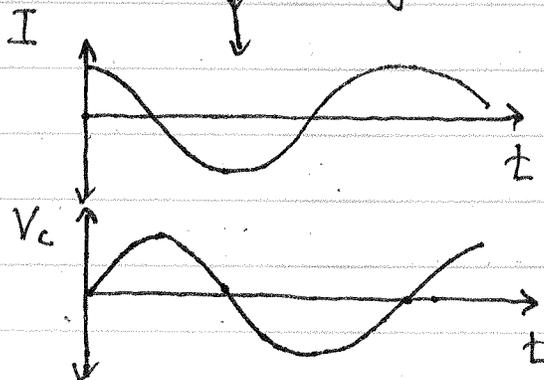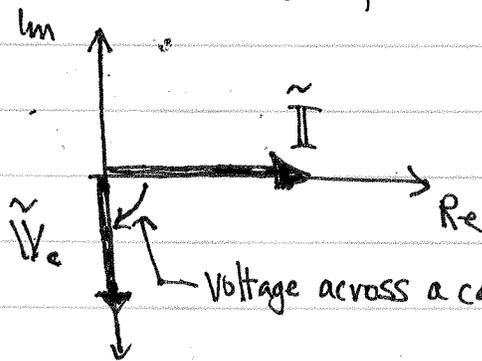



- Impedance of a resistor:  $V_R = IR$  Ohm's Law

or  $\rightarrow \tilde{V}_R = \tilde{I} R$


$$\tilde{Z}_R = R$$

Impedance of a resistor is real ... and equal to the resistance.

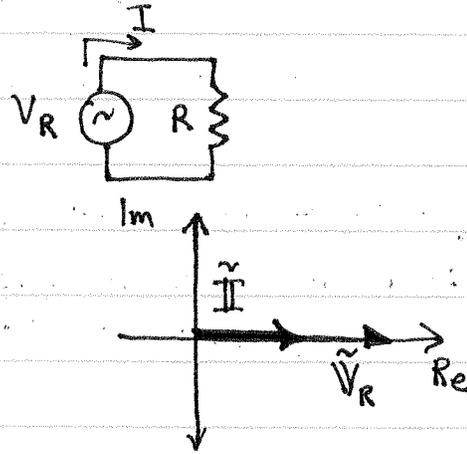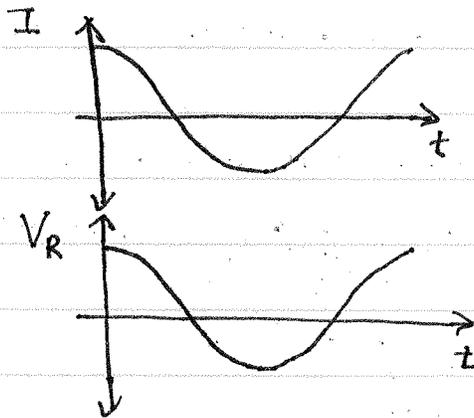Voltage and current are in-phase with each other.



- Impedance of an inductor:

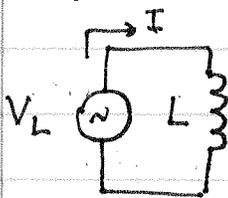

Kirchoff loop rule:  $V_L - L \frac{dI}{dt} = 0$



convert to complex notation:  $\tilde{V}_L = L \frac{d\tilde{I}}{dt}$

Since  $\tilde{I} = \tilde{I}_0 e^{j\omega t}$   $\frac{d\tilde{I}}{dt} = j\omega \tilde{I}_0 e^{j\omega t} = j\omega \tilde{I}$

Therefore ...  $\tilde{V}_L = j\omega L \tilde{I}$


$$\tilde{Z}_L = j\omega L$$

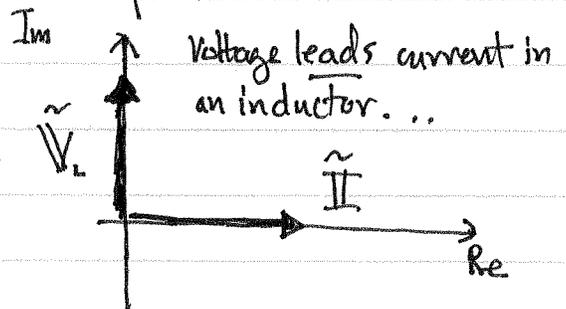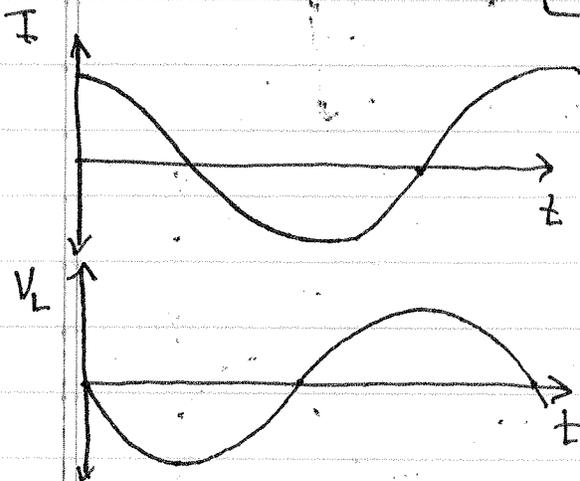Impedance of an inductor is small at low frequency and large at high frequency ... opposite of a capacitor.



Voltage leads current in an inductor ...

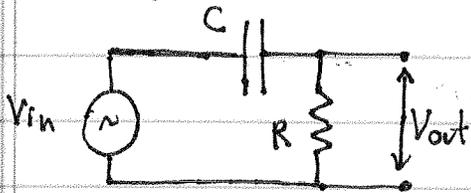Combining elements... RC High Pass Filter



Kirchoff loop rule using complex notation:

$$\tilde{V}_{in} - \tilde{I}Z_c - \tilde{I}R = 0$$

$$\text{or } \tilde{V}_{in} = \tilde{I}(\tilde{Z}_R + \tilde{Z}_C)$$

Impedance of the series combination of resistor and capacitor...

$$\tilde{Z}_{eff} = \tilde{Z}_R + \tilde{Z}_C = R - \frac{j}{\omega C}$$

$$\tilde{I} = \frac{\tilde{V}_{in}}{\tilde{Z}_{eff}} = \frac{\tilde{V}_{in}}{R - j/\omega C}$$

$$\tilde{V}_{out} = \tilde{V}_R = \tilde{I}R = \frac{R}{R - j/\omega C} \tilde{V}_{in}$$

Note similarity to voltage divider relation!

$$V_{out_0} e^{j\phi} e^{j\omega t} = \frac{R}{R - j/\omega C} V_{in_0} e^{j\omega t}$$

cancel all time dependence

$$V_{out_0} e^{j\phi} = \left( \frac{R}{R - j/\omega C} \right) V_{in_0}$$

phase shift between input and output voltages.

$$\frac{V_{out_0}}{V_{in_0}} e^{j\phi} = \frac{R}{R - j/\omega C} \cdot \frac{(R + j/\omega C)}{(R + j/\omega C)} = \frac{R^2 + jR/\omega C}{R^2 + (1/\omega C)^2} \div R^2$$

$$\frac{V_{out_0}}{V_{in_0}} e^{j\phi} = \frac{1 + j\omega RC}{1 + (\omega RC)^2}$$

To get  $\frac{V_{out_0}}{V_{in_0}}$ , take absolute value of complex quantity on right side...

$$\frac{V_{out0}}{V_{in0}} = \frac{\sqrt{1 + \left(\frac{1}{\omega RC}\right)^2}}{\left(1 + \left(\frac{1}{\omega RC}\right)^2\right)} \leftarrow \sqrt{\text{of sum of Re part squared plus Im part squared.}}$$


OR...  $\boxed{\frac{V_{out0}}{V_{in0}} = \frac{1}{\sqrt{1 + \left(\frac{1}{\omega RC}\right)^2}}}$  OR  $\frac{1}{\sqrt{1 + \left(\frac{f_0}{f}\right)^2}}$  where  $f_0 = \frac{1}{2\pi RC}$   
and  $f = \frac{\omega}{2\pi}$

To get phase shift ...  $\phi = \tan^{-1}\left(\frac{\text{Im}(\quad)}{\text{Re}(\quad)}\right)$

↑ right side of expression on previous page.

$$\boxed{\phi = \tan^{-1}\left(\frac{1}{\omega RC}\right)} \text{ or } \phi = \tan^{-1}\left(\frac{f_0}{f}\right)$$

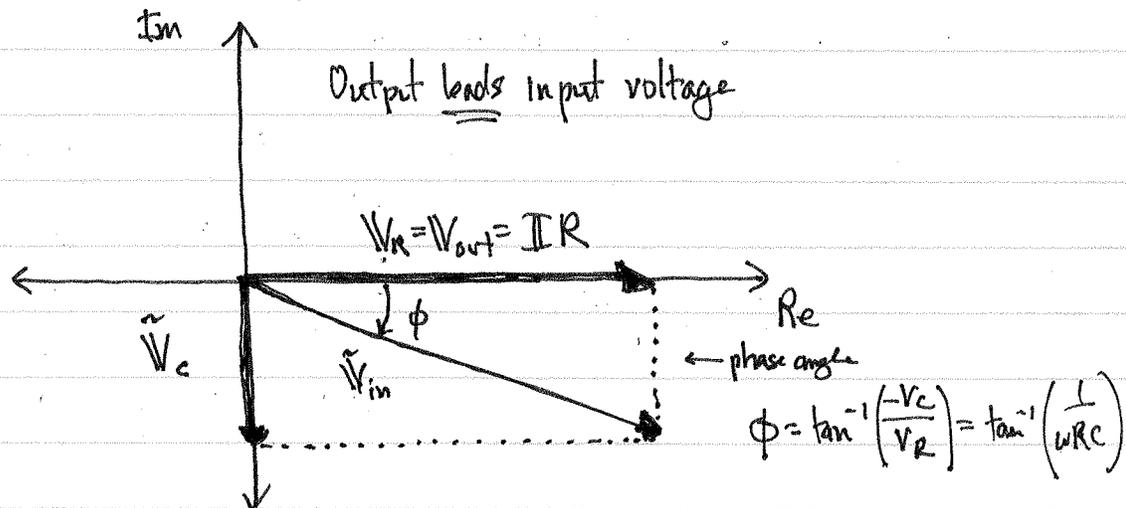• Phase diagram for RC High Pass Circuit :



Kirchoff's loop rule for complex phasors.  $\tilde{V}_{in} - \tilde{V}_c - \tilde{V}_R = 0$

or...  $\tilde{V}_{in} = \tilde{V}_c + \tilde{V}_R$  Pythagorus  $V_{in0}^2 = V_c^2 + V_R^2$


$$V_{in0} = \sqrt{I_0^2 \left(\frac{1}{\omega C}\right)^2 + I_0^2 R^2} = I_0 \sqrt{\left(\frac{1}{\omega C}\right)^2 + R^2}$$

↑ also  $V_{out0}$



magnitude of complex impedance.

$$V_{out0} = I_0 R = \frac{R}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} V_{in0} \text{ OR } \Rightarrow \frac{V_{out0}}{V_{in0}} = \frac{1}{\sqrt{1 + \left(\frac{1}{\omega RC}\right)^2}}$$

• RLC Series Resonant Circuit :

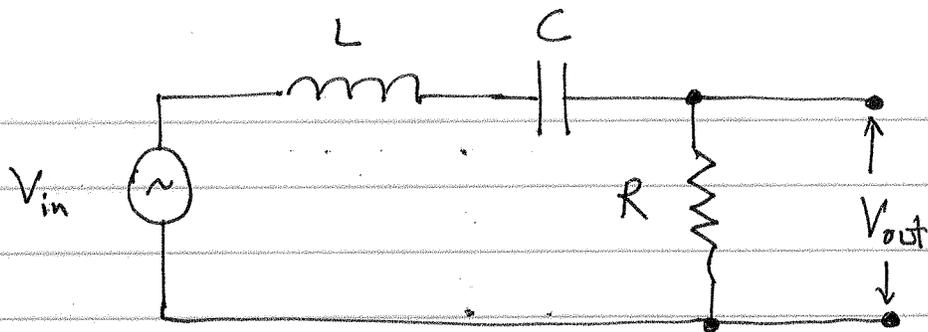

Phasor diagrams

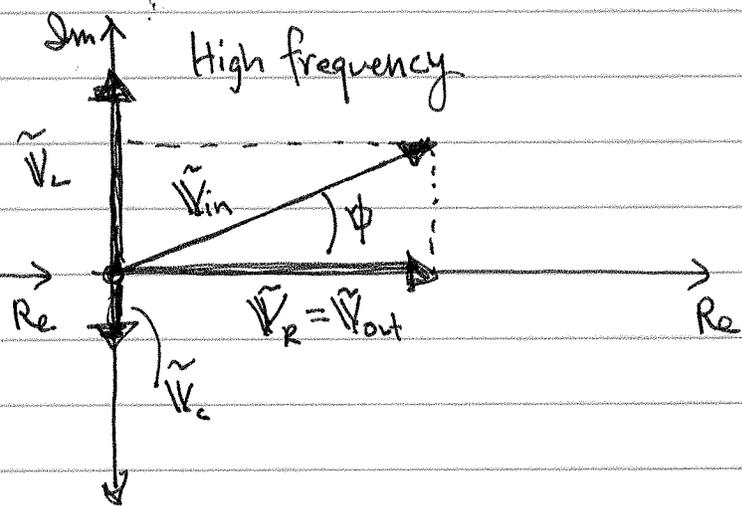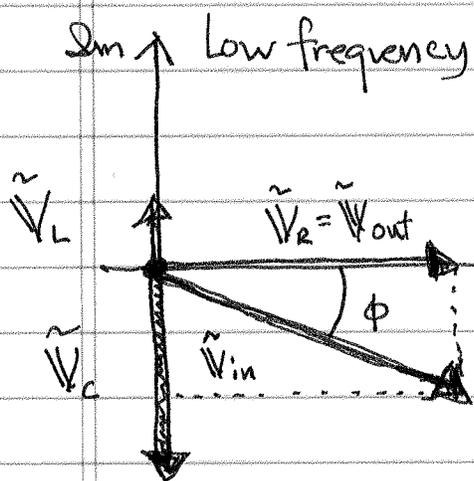

Kirchoff : 
$$\tilde{V}_{in} - (\tilde{V}_L + \tilde{V}_C + \tilde{V}_{R_{out}}) = 0$$

Use Pythagorean theorem to relate amplitudes of these quantities

$$V_{in} = \sqrt{(\omega L I_0 - \frac{1}{\omega C} I_0)^2 + R^2 I_0^2} = I_0 \sqrt{(\omega L - \frac{1}{\omega C})^2 + R^2}$$

$$V_{out} = V_R = I_0 R = \frac{R}{\sqrt{(\omega L - \frac{1}{\omega C})^2 + R^2}} \cdot V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{R}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} = \frac{1}{\sqrt{1 + \frac{\omega^2 L^2}{R^2} (1 - \omega^2 LC)^2}}$$

• Resonant frequency  $\omega_0 = \frac{1}{\sqrt{LC}}$   $f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{LC}}$

$$\frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{1 + \left(\frac{\omega_0 L}{R}\right)^2 \left(\frac{\omega}{\omega_0}\right)^2 \left(1 - \frac{\omega_0^2}{\omega^2}\right)^2}}$$

define the "quality factor"  $Q_0 \equiv \frac{\omega_0 L}{R}$

→ sharpness of the resonance peak


$$\frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{1 + Q_0^2 \left(\frac{\omega}{\omega_0}\right)^2 \left(1 - \left(\frac{\omega_0}{\omega}\right)^2\right)^2}}$$

• Phase shift (see phasor diagram):



$$\phi = \tan^{-1} \left( \frac{I_0 \left( \frac{1}{\omega C} - \omega L \right)}{I_0 R} \right) = \tan^{-1} \left[ \frac{1}{\omega R C} - \frac{\omega L}{R} \right]$$

can also be written as...
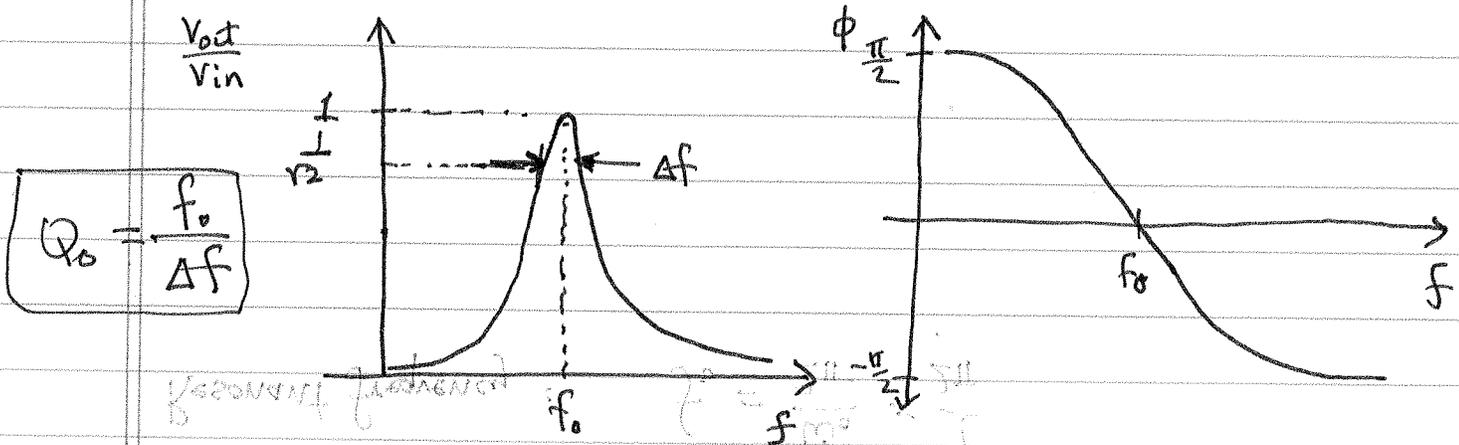
$$\phi = \tan^{-1} \left[ Q_0 \left( \frac{\omega}{\omega_0} \right) \left( \left( \frac{\omega_0}{\omega} \right)^2 - 1 \right) \right]$$



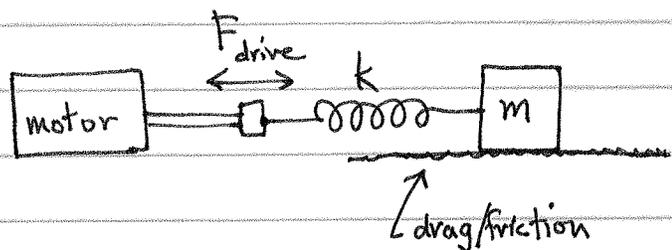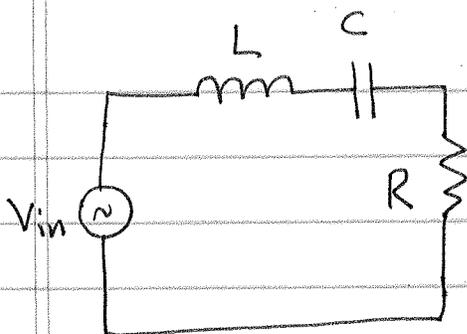• Mechanical Analog of LRC Resonant Circuit



Newton's 2<sup>nd</sup> Law

$$V_{in} - L \frac{dI}{dt} - \frac{Q}{C} - IR = 0 \quad F_{drive} - kx - Dv = ma$$

Or...  $V_{in} - \frac{1}{C} Q - IR = L \frac{dI}{dt}$

↑  
drag force  
D = drag coefficient

$$Q \longleftrightarrow x$$

$$I = \frac{dQ}{dt} \longleftrightarrow V = \frac{dx}{dt}$$

$$\frac{dI}{dt} \longleftrightarrow a = \frac{dv}{dt}$$

$$L \longleftrightarrow m$$

$$\frac{1}{C} \longleftrightarrow k$$

$$V_{in} \longleftrightarrow F_{drive}$$

$$R \longleftrightarrow D$$

Resonant freq.  $\omega_0 = \frac{1}{\sqrt{LC}} \longleftrightarrow \omega_0 = \sqrt{\frac{k}{m}}$