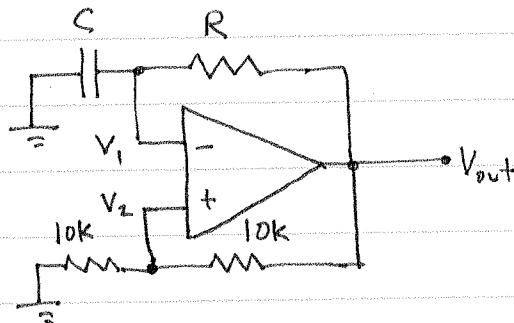


Notes on Clocks and Oscillators

- Relaxation Oscillator using an Op-Amp as a "comparator" or "Schmitt trigger". See Horowitz and Hill, p. 285.



Output of op-amp will swing from  $+V_{cc}$  to  $-V_{cc}$  depending on whether  $V_2 > V_1$  or  $V_2 < V_1$ .

Circuit has an unstable equilibrium:  $V_1 = V_2 = V_{out} = 0$  no charge on  $C$ .


Consider a small perturbation ...  $V_2 \rightarrow +\epsilon$

Because of large open-loop gain  $V_{out} \rightarrow +V_{cc}$  and  $V_2 \rightarrow \frac{+V_{cc}}{2}$


because of the voltage divider with 10k resistors.

Current flows through negative feedback network, charging capacitor.

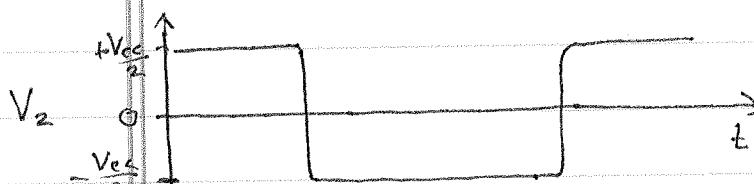$V_1$  increases on RC timescale until  $V_1 \geq \frac{+V_{cc}}{2}$  when the op-amp comparator swings its output to  $-V_{cc}$  ...



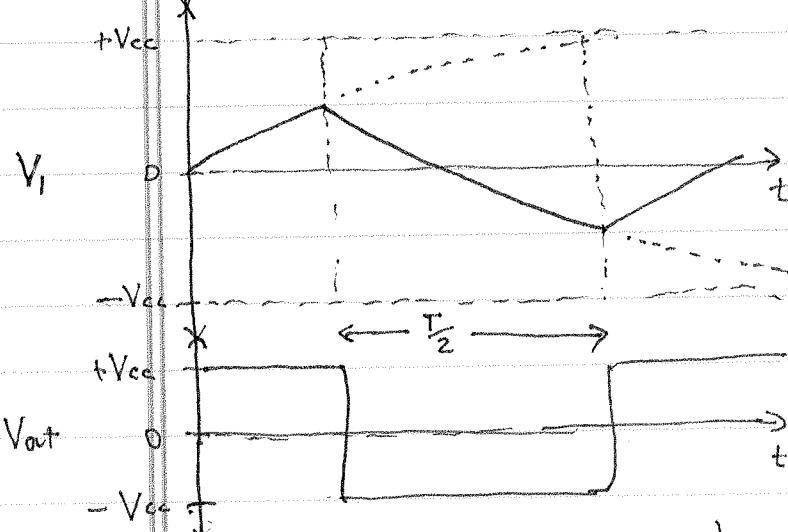In time  $\frac{T}{2}$  (half the "clock" period)  
 $V_1$  decays toward  $-V_{cc}$  from  $\frac{+V_{cc}}{2}$  to  $-\frac{V_{cc}}{2}$   
... ending up at  $\frac{1}{3}$  of its initial voltage difference with respect to  $-V_{cc}$ .




$$\text{So } e^{-\frac{T}{2RC}} = \frac{1}{3}$$

$$\text{or } T = (2 \ln 3) RC$$


$$T \approx 2.2 RC$$

- Relaxation Oscillator using Inverter Gates (see Horowitz and Hill, p. 285).

→ "Inverter Clock"

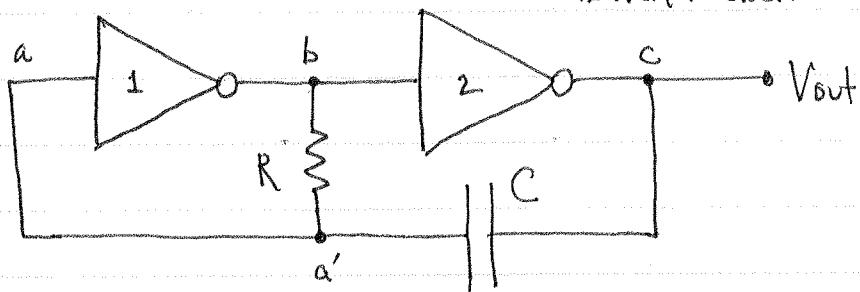

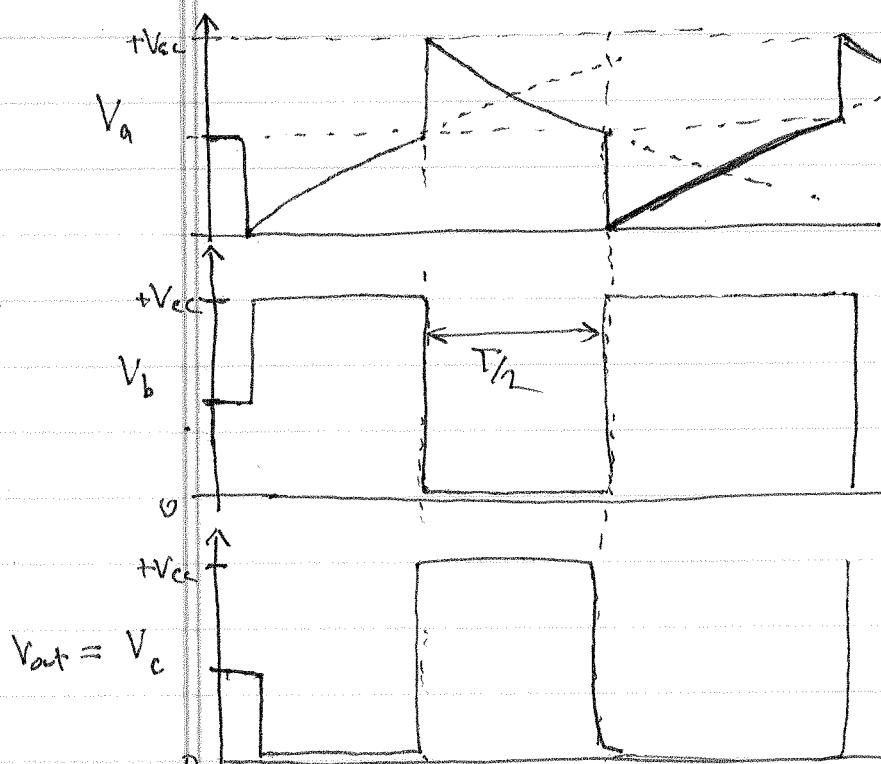- (1) This circuit has an unstable equilibrium at  $V_a = V_b = V_c = \frac{V_{cc}}{2}$ .
- (2) Consider a small perturbation at b such that  $V_b = \frac{V_{cc}}{2} + \epsilon$
- (3) Inverter #2 output will swing LO. The initial low-going pulse will couple through Capacitor C, pulling  $V_a$  LO and inverter #1 output will swing HI reinforcing the perturbation.
- (4) Current will flow from b to a' and charge the capacitor. When  $V_a = V_{a'} = \frac{V_{cc}}{2}$  inverter #1 output will swing LO, inverter #2 output will swing HI, pulling  $V_a$  HI




In time  $\frac{T}{2}$ ,  $V_a$  decays from  $+V_{cc}$  to  $\frac{V_{cc}}{2}$  ... ending up at  $\frac{1}{2}$  its initial voltage (with respect to LO).

$$\text{So } e^{-\frac{T}{2RC}} = \frac{1}{2}$$

$$\text{or } T = 2 \ln 2 RC$$

$$T \approx 1.4 RC$$

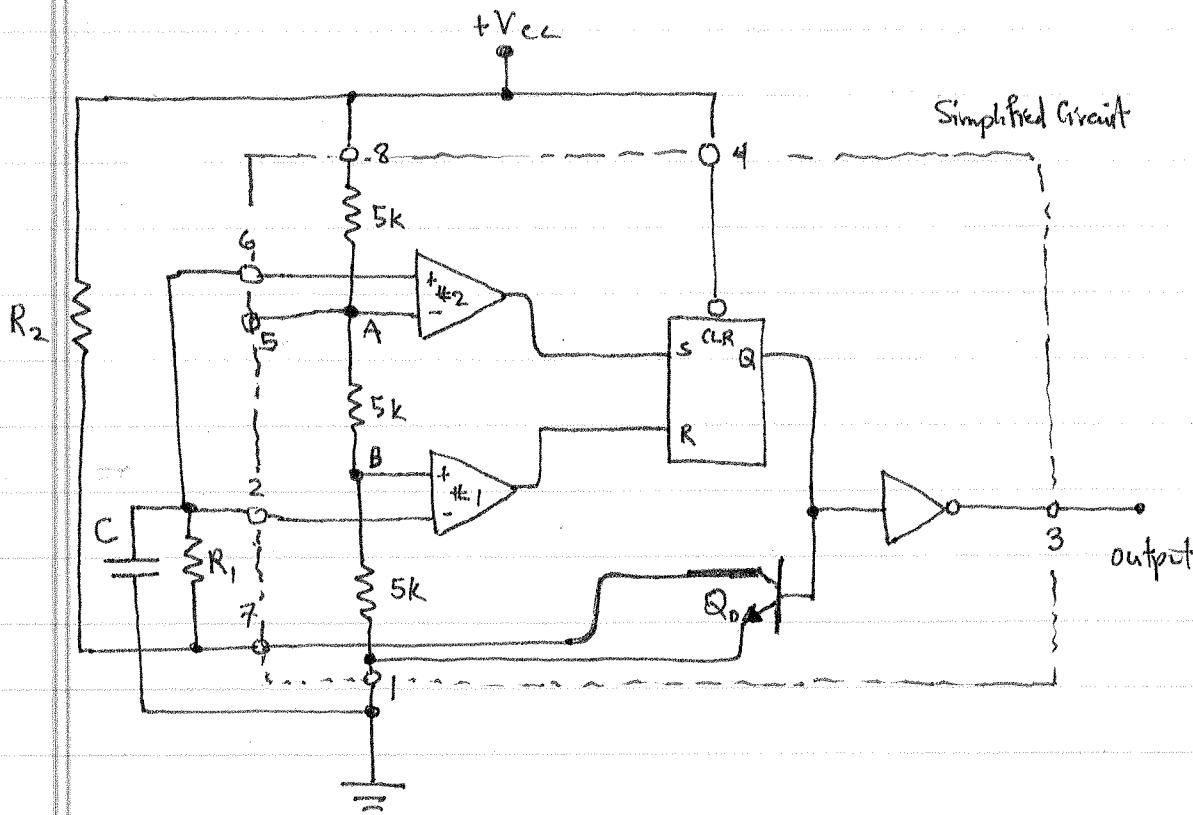- Using the 555 Timer Chip to generate a digital clock:



This circuit has


- 1) Voltage divider
- 2) RC charging/discharging circuit
- 3) transistor used as a switch
- 4) Op-amps used as comparators
- 5) Logic gate ... inverter
- 6) Flip-flop

S	R	Q
0	0	memory
0	1	0
1	0	1
1	1	undesirable

→ Nice summary of the course!

Note that  $V_A = \frac{2}{3} V_{cc}$  and  $V_B = \frac{1}{3} V_{cc}$ . These reference voltage levels are compared to the voltage on pins 2 and 6... voltage across the capacitor!

- Start with no charge on capacitor  $V_2 = V_6 = 0$
- $V_6 < V_A$  ... comparator #2 is LO ...  $S = 0$  on FF. } reset
- $V_2 \leq V_B$  ... comparator #1 is HI ...  $R = 1$  on FF
- Output of FF,  $Q = 0$  ...  $V_{out} = 1/HI$
- Transistor is OFF
- Capacitor charges through  $R_1 + R_2$ .
- When  $V_2 = V_6 = \frac{1}{3}V_{cc}$  then  $R = 0$ . FF is in memory state ... no change in output
- When  $V_2 = V_6 = \frac{2}{3}V_{cc}$  then  $S = 1 / R = 0$  FF is in ~~set~~ set state
- Output of FF  $Q = 1$  ...  $V_{out} = 0/LO$
- Transistor is ON
- Capacitor discharges through  $R_1$  ...  $S \rightarrow 0$  memory
- When  $V_2 = V_6 = \frac{1}{3}V_{cc}$  ...  $R \rightarrow 1$  ... reset ... transistor off...  $V_{out} = 1/HI$
- capacitor charges

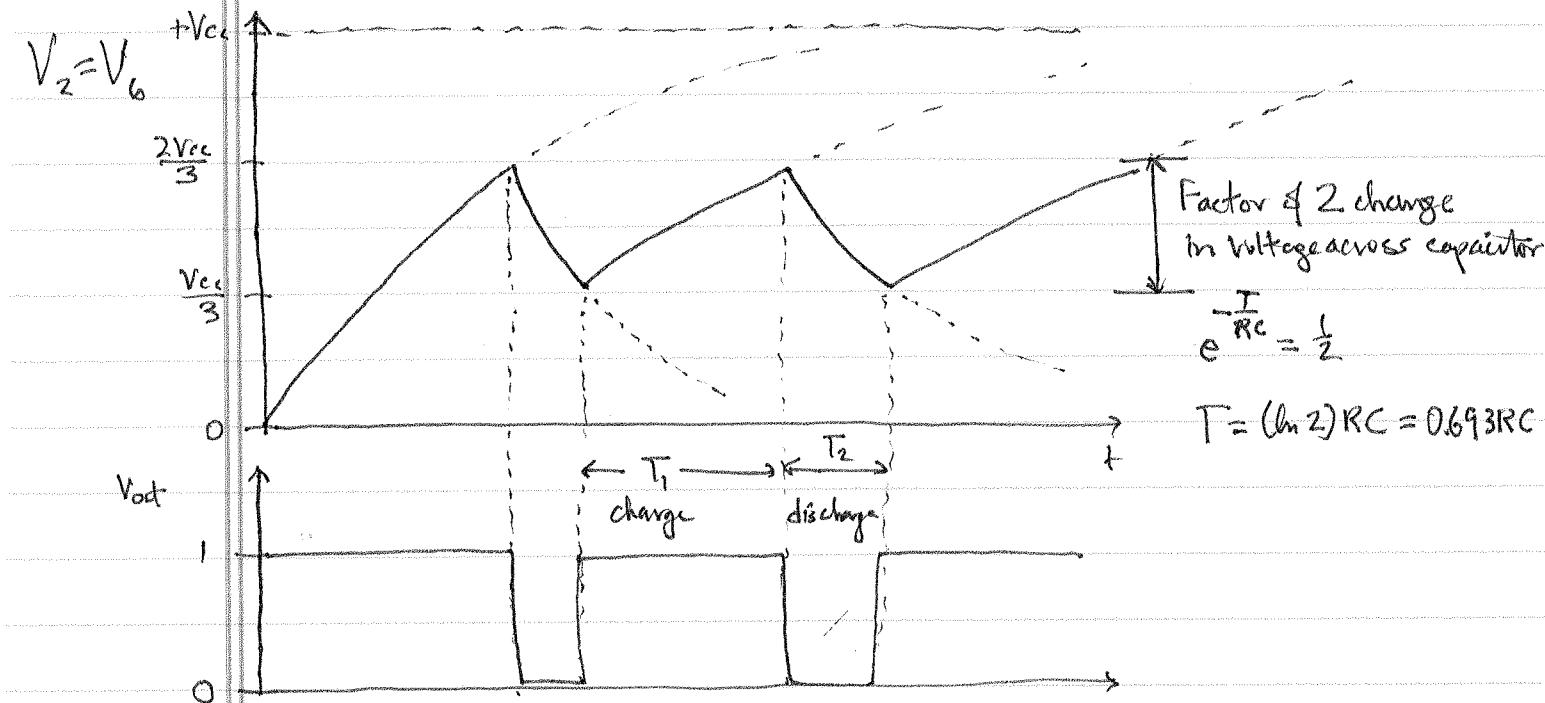


$$T_1 = 0.69 (R_1 + R_2) C$$

$$T_2 = 0.69 R_1 C$$

- Positive Feedback and the Wien Bridge Oscillator

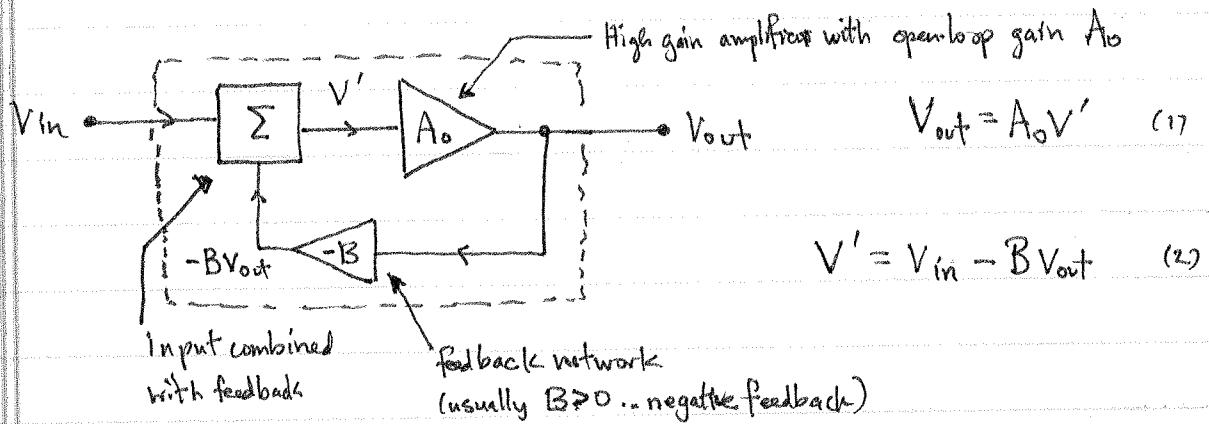Block diagram for amplifier employing feedback



Combine equations (1) + (2)

$$V_{out} = A_o V_{in} - A_o B V_{out}$$

or...

$$V_{out} = \frac{A_o}{(1 + A_o B)} V_{in}$$

If  $B > 0$  ... negative feedback ... things are fine.

But, if  $B < 0$ , then things go haywire when  $|B| = \frac{1}{A_o}$   
→ positive feedback!! even if  $V_{in}$  is not present

Since  $B$  can be frequency-dependent this condition might pertain

(a) at one (or a narrow range of) frequency (-ies)

→ sinusoidal oscillations at that frequency


(b) over a wide range of frequencies

→ distorted or perhaps square-wave oscillations.

Example: The Wien Bridge Oscillator.


- Wien Bridge Oscillator

Start with a non-inverting opamp circuit

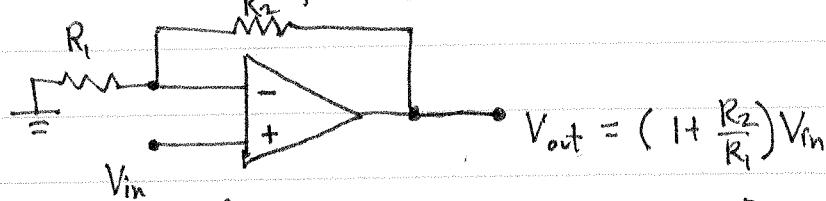

Consider this to be our high gain amp with  $A_o = \left(1 + \frac{R_2}{R_1}\right)$

Now add positive feedback

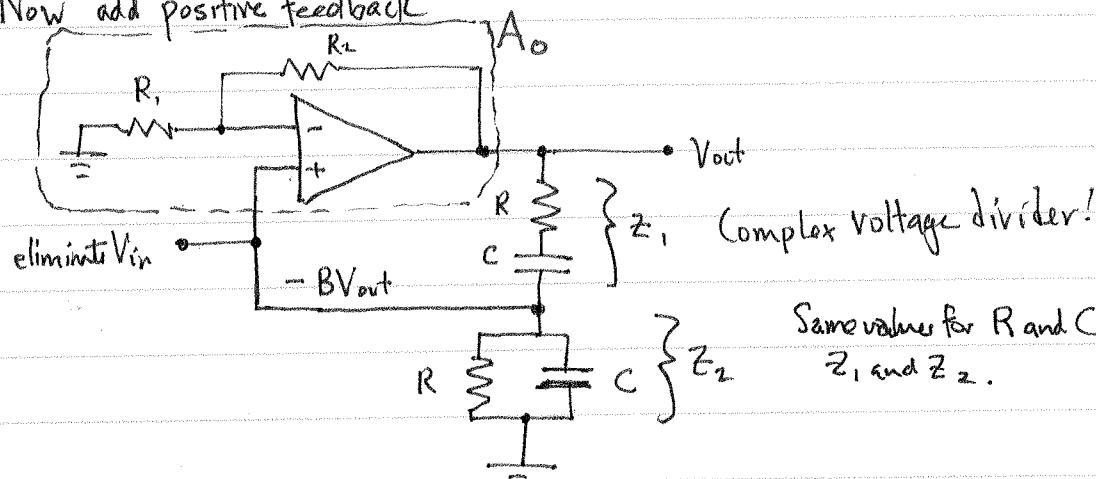

$$-BV_{out} = \frac{z_2}{z_1 + z_2} V_{out} \quad \text{or..} \quad B = \frac{-z_2}{z_1 + z_2}$$

$$\text{or} \quad B = \frac{-1}{\left(\frac{z_1}{z_2}\right) + 1}$$

$$z_1 = R - \frac{j}{\omega C} \quad z_2^{-1} = \frac{1}{R} + j\omega C$$

$$\text{so..} \quad \frac{z_1}{z_2} = \left(R - \frac{j}{\omega C}\right) \left(\frac{1}{R} + j\omega C\right) = 2 + j\left[\omega RC - \frac{1}{\omega RC}\right]$$

$$\text{and } B = \frac{-1}{3 + j\left[\omega RC - \frac{1}{\omega RC}\right]} \quad \text{Will get instability/oscillation threshold when}$$

$$B \text{ is negative and real.. when } \omega RC - \frac{1}{\omega RC} = 0$$


$$\text{or..} \quad \cancel{\omega RC - \frac{1}{\omega RC} = 0} \quad \cancel{\Rightarrow \omega^2 = \frac{1}{4RC^2}}$$

$$\omega = \frac{1}{RC} \quad f = \frac{1}{2\pi RC}$$

$$\text{AND then } B = -\frac{1}{3} \dots \text{Also need } |A_o B| > 1 \text{ so.. } A_o = 3$$

$$\text{or..} \quad \frac{R_2}{R_1} \geq 2 \text{ at threshold}$$

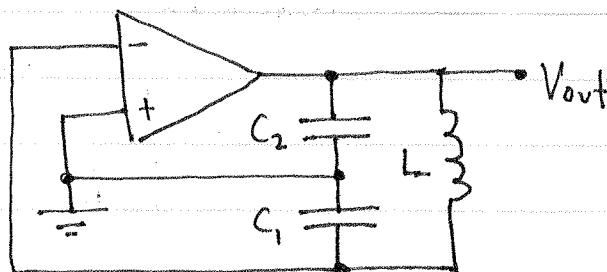- Example of an LC oscillator using an Op Amp : Colpitts Oscillator



The feedback network is an LC "tank" circuit with a resonant frequency at

$$\omega_0 = \frac{1}{\sqrt{LC_{eq}}}$$


$C_{eq}$  is the equivalent capacitance of  $C_1$  and  $C_2$  in series.

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

so..


$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC_{eq}}} = \frac{1}{2\pi} \sqrt{\frac{C_1 + C_2}{LC_1 C_2}}$$

Redrawing feedback network

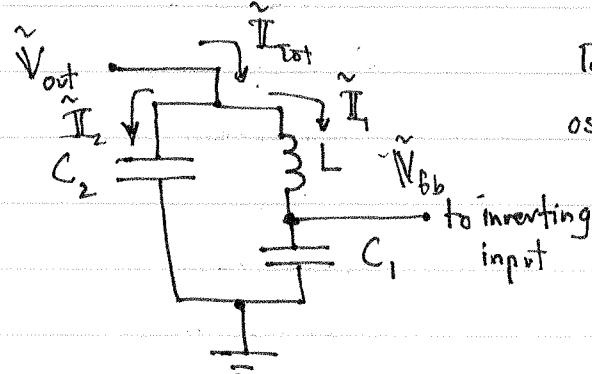

To make feedback result in oscillations, the signal to inverting input of op-amp should be  $180^\circ$  out of phase with  $V_{out}$ ... positive feedback.

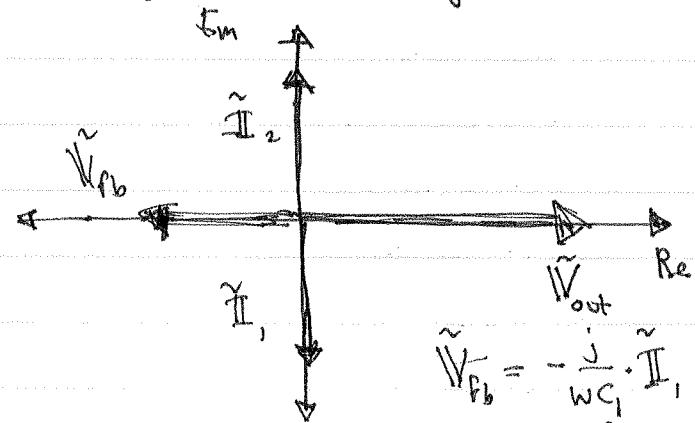Phasor diagram for currents/voltage at resonance.



$$\tilde{I}_2 = \frac{\tilde{V}_{out}}{Z_2} = j\omega C_2 \tilde{V}_{out}$$

$$\tilde{I}_1 = \frac{\tilde{V}_{out}}{Z_1} = \frac{-j\tilde{V}_{out}}{(\omega L - \frac{1}{\omega C_1})}$$

$$\text{at resonance } \tilde{I}_{tot} = \tilde{I}_1 + \tilde{I}_2 = 0 \quad (Q \rightarrow \infty)$$

$\tilde{V}_{fb} = -j \cdot \tilde{I}_1$ ,  $90^\circ$  behind  $\tilde{I}_1$ , and  $\tilde{I}_1$  is  $90^\circ$  behind  $\tilde{V}_{out}$

- Crystal Oscillators: Quartz crystals can have mechanical (vibrational) resonances with very high quality factors ...  $Q > 10^5$ . The resonance can be coupled to an electric circuit because of the piezoelectric effect where the mechanical strain associated with the crystal's vibration results in voltage across the crystal.

Circuit symbol for crystal 

$C_p \leftarrow$  due to electrodes on crystal

Electronic equivalent

$L \longleftrightarrow$  inertial component of oscillation



$\frac{1}{C_s} \longleftrightarrow$  elastic component of oscillation



$R \quad L \quad C_s \leftarrow C_s \ll C_p$

small ... high Q

oscillator  
Some circuits using crystal

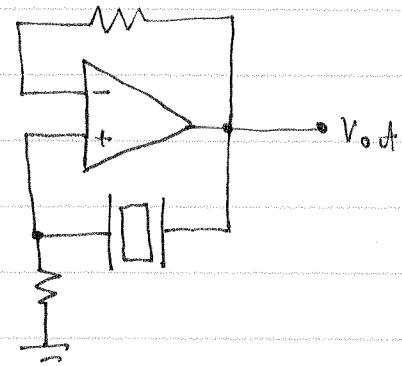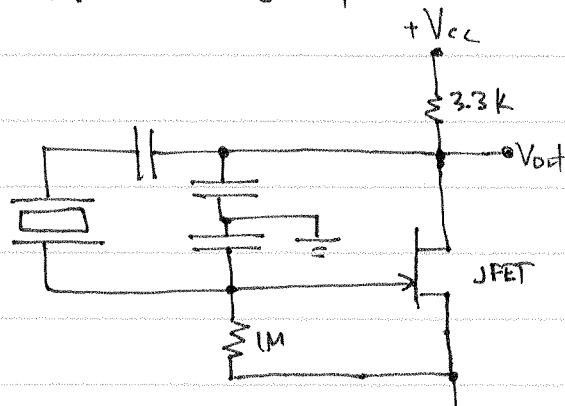

CMOS inverter-based crystal oscillator

