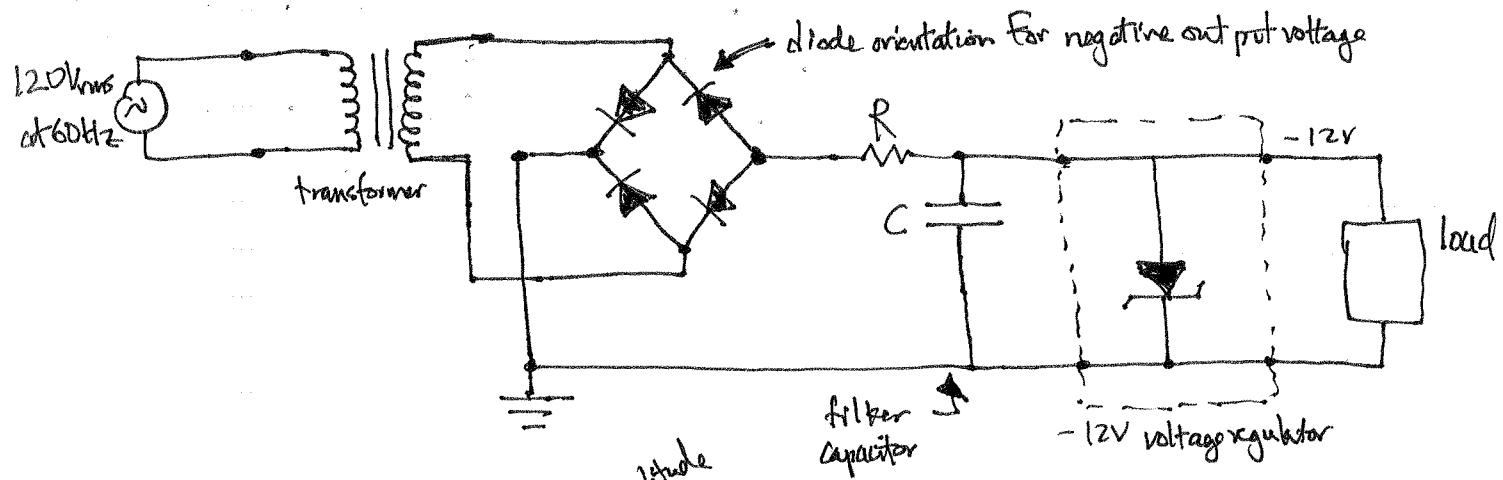


PHYSICS 220 : Physical Electronics Problem Set #3 SOLUTIONS

Simpson Ch.4 : 23, 25, 26, ~~28~~, Ch.5 : 8, 10, 11, 12

Simpson, chapter 4 :

- [23] Sketch a full-wave rectifier circuit to produce a -12 V DC output.



- This ~~is not~~ primary voltage amplitude on the transformer is $V_p = 120V \cdot \sqrt{2} = 170V$
- We want the secondary to be $V_s \geq 12V + 2 \times 0.6V = 13.2V$

Since there are two forward-biased diodes between output and ground in each half cycle.

So... the turns ratio on the transformer should be about...

$$\frac{N_s}{N_p} > \frac{13.2}{170} = 0.0776 \quad \text{or..} \quad \frac{N_p}{N_s} \leq 12.9$$

Choose $\boxed{\frac{N_p}{N_s} = 12}$ or $\frac{N_s}{N_p} = 0.0833$

- The filter capacitor has to be big enough to reduce the ripple to acceptable levels under load conditions. If, for example, we want to draw 100 mA, then in $\frac{1}{120\text{ Hz}} = 8.3\text{ ms}$

(the ~~peak~~ period of the ripple), the voltage on the filter capacitor will decrease by approximately...

$$\Delta V = \frac{I_{\text{load}} \Delta t}{C} \quad \text{. For the ripple to be less than 5% of the DC output level under loaded conditions... we need} \quad C > \frac{I_{\text{load}} \Delta t}{0.05 V_{\text{DC}}} = \frac{0.1A \cdot 8.3}{0.05 \cdot 12V} = 1.4 \times 10^{-3} F$$

- The filter resistor R should be small so the DC output does not drop, under loaded conditions


$$V_{\text{out}} = \frac{R_{\text{load}}}{R + R_{\text{load}}} \cdot V_{\text{in}}$$

$$14,000 \mu F$$

$$\text{If } \frac{V_{\text{out}}}{V_{\text{in}}} = 0.95, \text{ then...} \quad \frac{R}{R_{\text{load}}} + 1 \leq \frac{1}{0.95} \quad \text{or} \quad R \leq 0.053 R_{\text{load}} = 0.053 \cdot \frac{12V}{1A} = \underline{\underline{6.3 \Omega}}$$

25



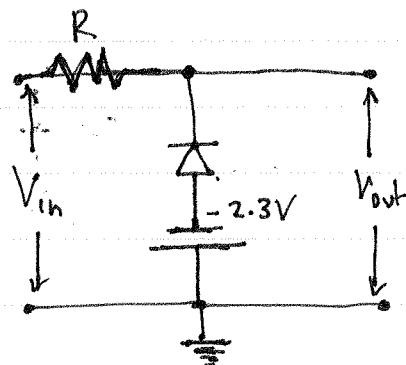
Diode clipping circuit to clip off negative-going pulses at -3.0 V .



When the input goes more negative than -3.0 V , the diode is forward-biased and current flows so that the portion of V_{in} that is more negative than -3 V appears across the resistor R , and not across the output.

26

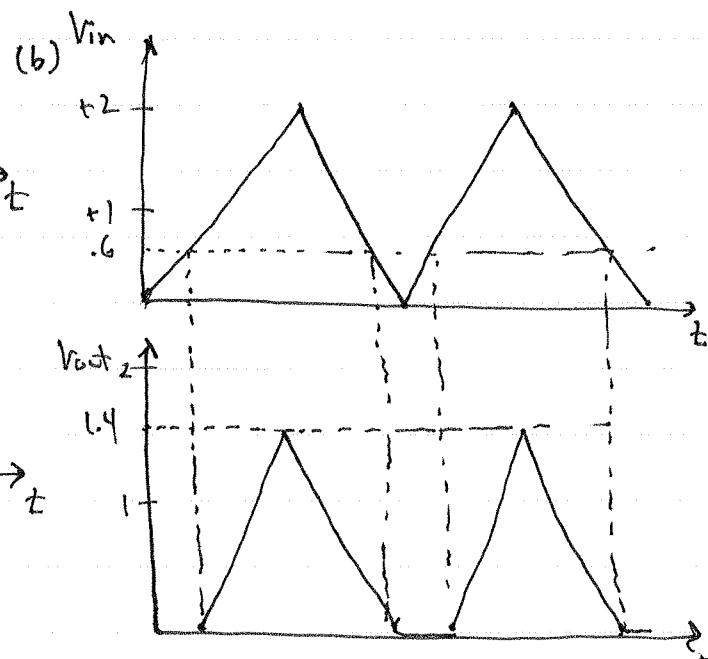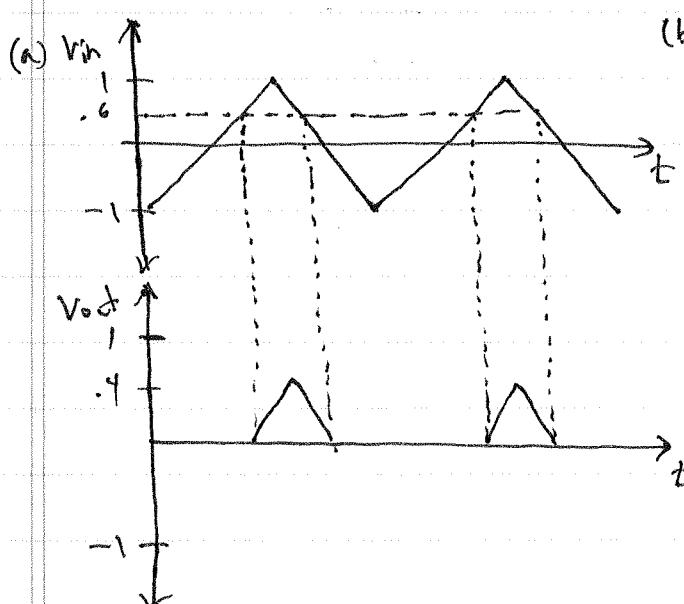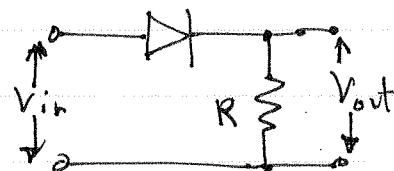Sketch the output voltage, ~~when~~ for the following circuit and input waveforms.




Simpson, chapter 5:

[8]

Sketch a graph of collector current vs. base-emitter voltage for a silicon transistor. Repeat for base current vs. base-emitter voltage. Use $\beta = 50$.


The base-emitter is a pn junction ... $\rightarrow I_B$ vs. V_{BE} looks like a diode.

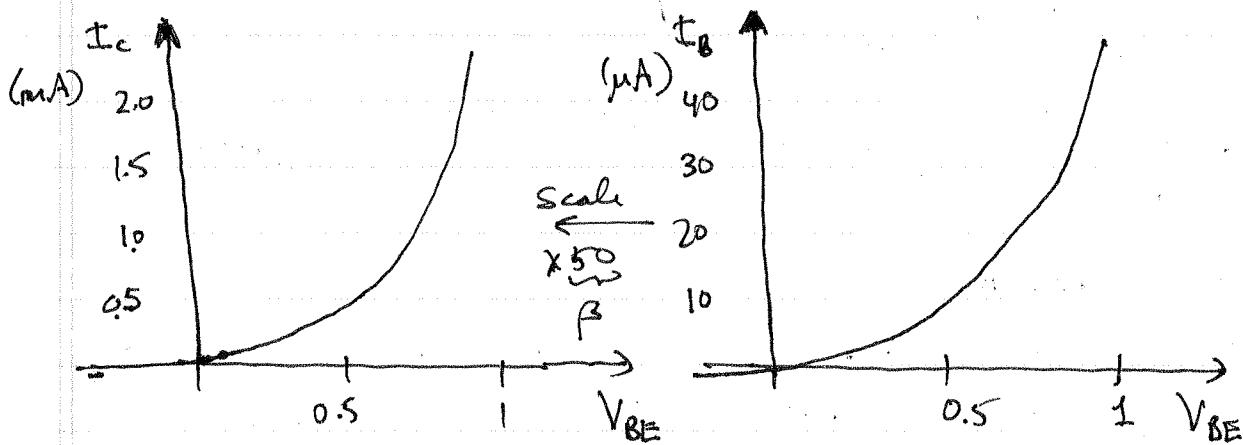And the transistor maintains (approximately) $I_C = \beta I_B$ so...




[15]

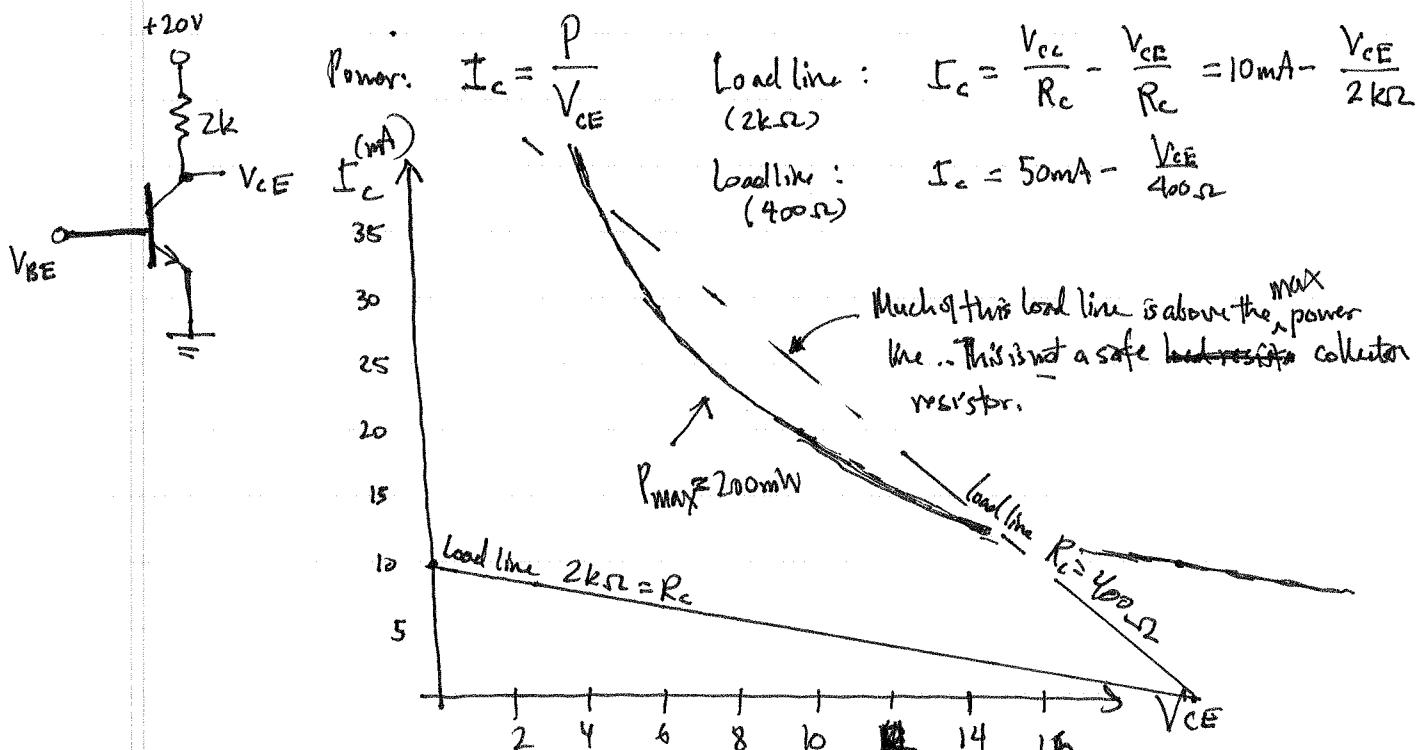Consider a transistor with $P_{max} = 200\text{mW}$ and a 20V power supply. Plot the max power curve on a graph of I_c vs. V_{CE} . Also draw the load line for a $2\text{k}\Omega$ collector resistor.



11

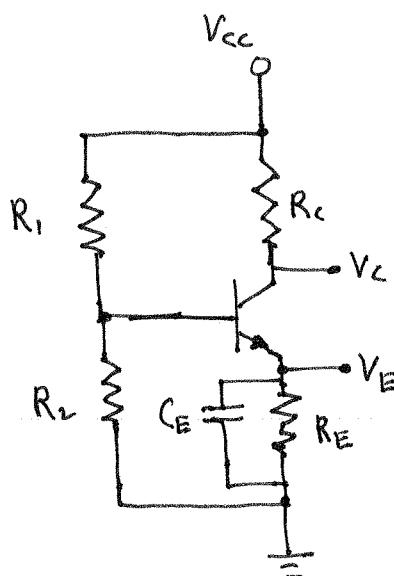Calculate I_c and V_{CE} . The transistor has a β of 100.



- The bypass capacitor on the emitter does not affect the DC quiescent operation of the transistor

- Base voltage is output of a voltage divider

$$V_B = \frac{R_2}{R_1 + R_2} \cdot V_{CC} = \frac{1}{5} \cdot 15V = \underline{\underline{3.0V}}$$

- Emitter is one forward-biased diode drop lower than this

$$V_E = V_B - 0.7V = \underline{\underline{2.3V}}$$

- The current through the emitter resistor is therefore $I_E = \frac{V_E}{R_E} = \frac{2.3V}{1k\Omega} = \underline{\underline{2.3mA}}$

- The collector current is approximately equal to the emitter current when $\beta \gg 1$.

$$\boxed{I_c \approx 2.3mA}$$

- The collector voltage is $V_c = V_{CC} - I_c R_c = 15V - 2.3mA \cdot 2k\Omega = 15V - 4.6V$

$$V_c = 11.4V$$

- So the collector-to-emitter voltage is...


$$V_{CE} = V_c - V_E = 11.4V - 2.3V = \boxed{9.1V}$$

- Check to see that I_B is much less than current in R_2 ... otherwise voltage divider is loaded down...

$$I_B \approx \frac{I_c}{\beta} \approx 23\mu A$$

and $I_2 = \frac{V_B}{R_2} = \frac{3.0V}{10k\Omega} = \underline{\underline{333\mu A}}$ much greater... check ✓

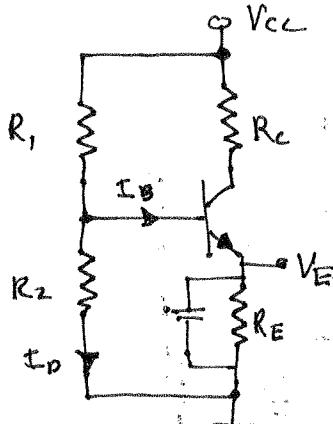- 12 Calculate R_1 and R_2 if $I_D = 20I_B$. The transistor is silicon and has $\beta = 100$. $V_E = 1V$.



• Knowing that the emitter voltage is 1V, we can find the emitter current.

$$I_E = \frac{V_E}{R_E} = \frac{1V}{500\Omega} = 2.0 \text{ mA}$$

• Since $\beta \gg 1$ $I_C \approx I_E = 2.0 \text{ mA}$

• The base current is, therefore, $I_B = \frac{I_C}{\beta} \approx 20 \mu\text{A}$

• The base voltage is $V_B = V_E + 0.7V = 1.7V$

• The current I_D , in resistor R_2 is $I_D = V_B/R_2$ and we want this to be 20x larger than I_B ... so...

$$R_2 = \frac{1.7V}{400\mu\text{A}} = [4.25 \text{ k}\Omega]$$

• To get $V_B = 1.7V$ from the voltage divider formed from R_1 and R_2 ...

$$V_B = \frac{R_2}{R_1 + R_2} \cdot V_{cc} \quad \text{solve for } R_1 \dots$$

$$\frac{R_1 + R_2}{R_2} = \frac{V_{cc}}{V_B} \quad \text{or} \quad \frac{R_1}{R_2} + 1 = \frac{V_{cc}}{V_B}$$

$$\text{or... } R_1 = R_2 \left[\frac{V_{cc}}{V_B} - 1 \right] = 4.25 \text{ k}\Omega \left[\frac{15V}{1.7V} - 1 \right] \\ = [33.25 \text{ k}\Omega]$$